

Digital Circuits and Systems

Spring 2015

Week 1 Module 2

*Shankar Balachandran**


Associate Professor, CSE Department
Indian Institute of Technology Madras

*Currently a Visiting Professor at IIT Bombay

Binary Switch




(a) Two states of a switch

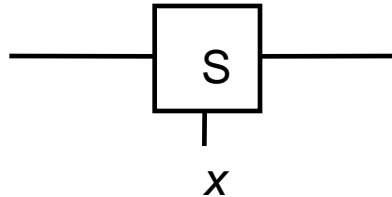

(b) Symbol for a switch


A Light Controlled by a Switch

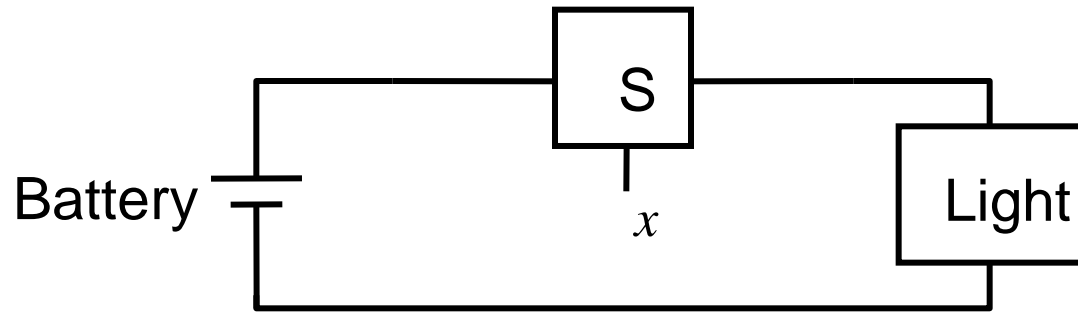


Simple connection to a battery

Two Basic Functions

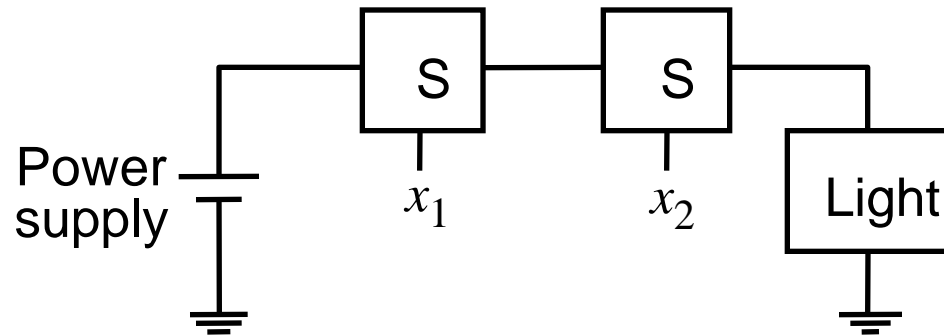
(a) The logical
AND function
(series
connection)



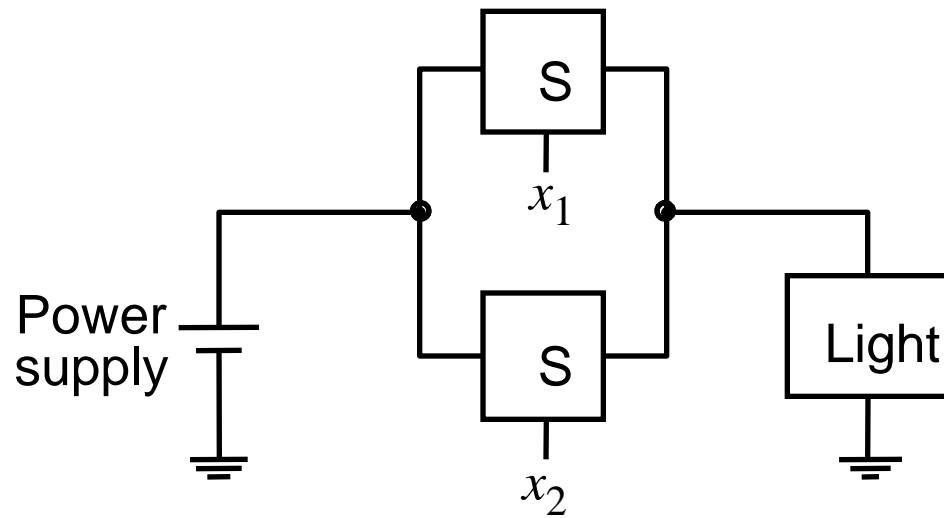
(b) The logical
OR function
(parallel
connection)



A Series Parallel Circuit

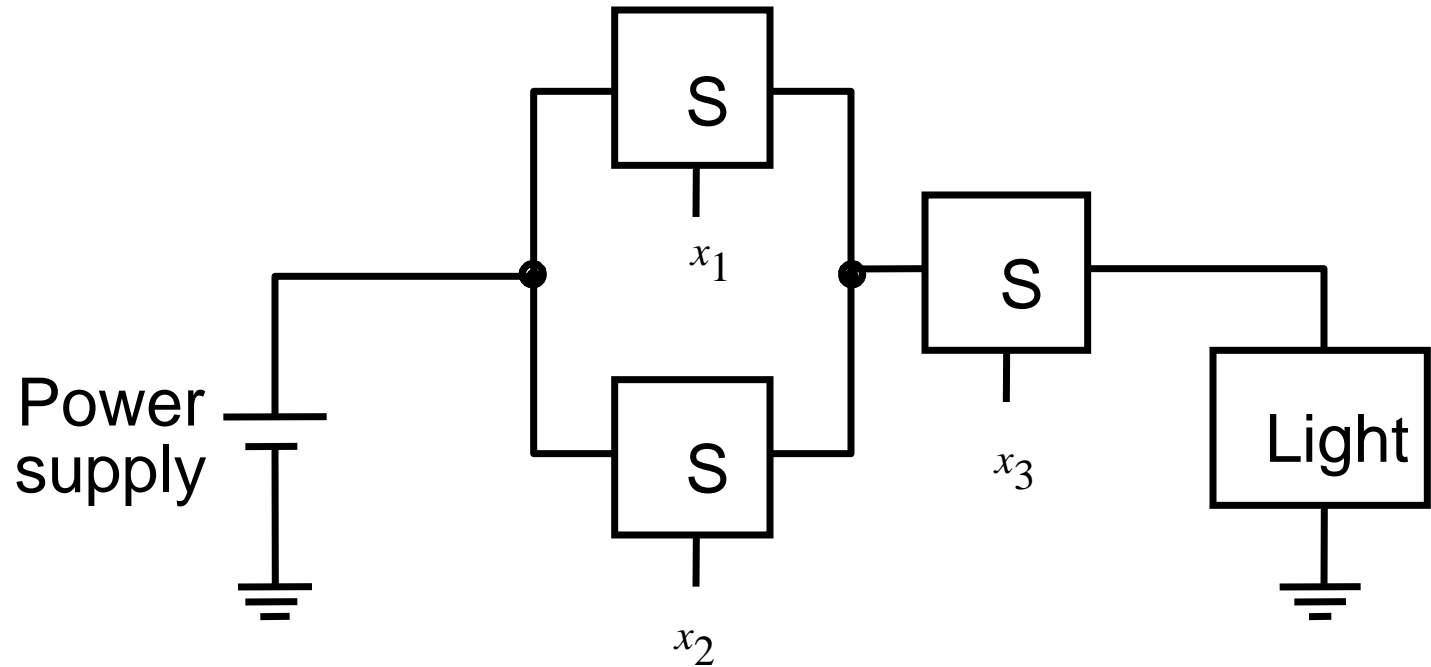

An Inverting Circuit

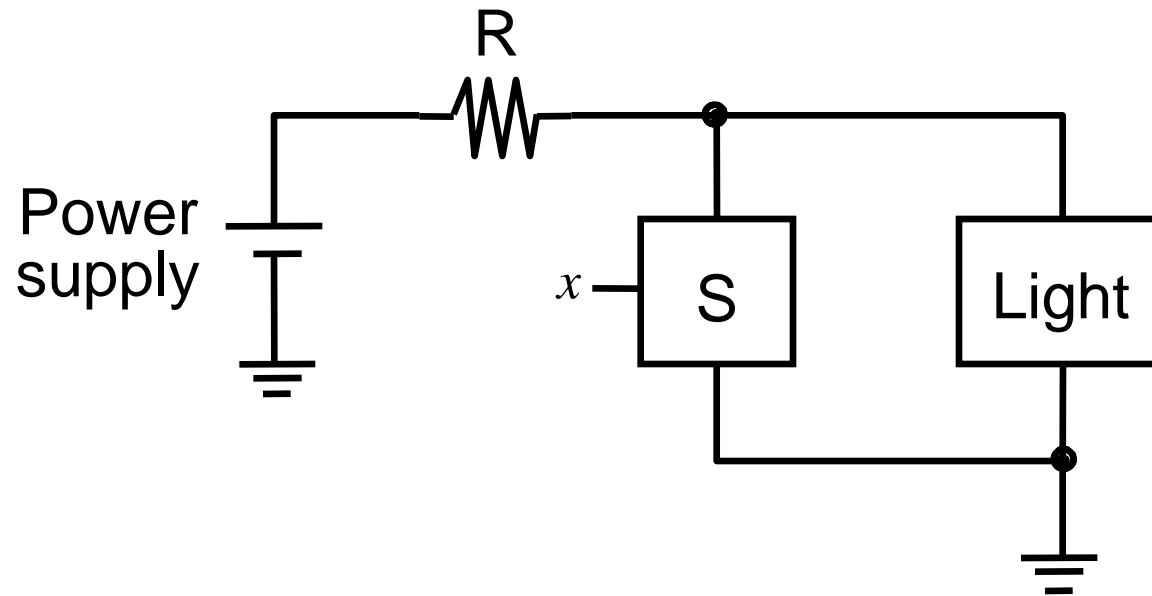

Truth Table

x_1	x_2	$x_1 \bullet x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

AND

OR

Truth Table of 3-Input AND and OR Operations

x_1	x_2	x_3	$x_1 \bullet x_2 \bullet x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth Table of 3-Input AND and OR Operations

x_1	x_2	x_3	$x_1 \bullet x_2 \bullet x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Symbols

■ AND


- Dot (\bullet)
- Imagine it to be like multiplication
- Example $x \bullet y$
- Called “x and y”

■ OR

- Plus ($+$)
- Imagine it to be like addition
- Example $x + y$
- Called “x or y”


NOT Operation

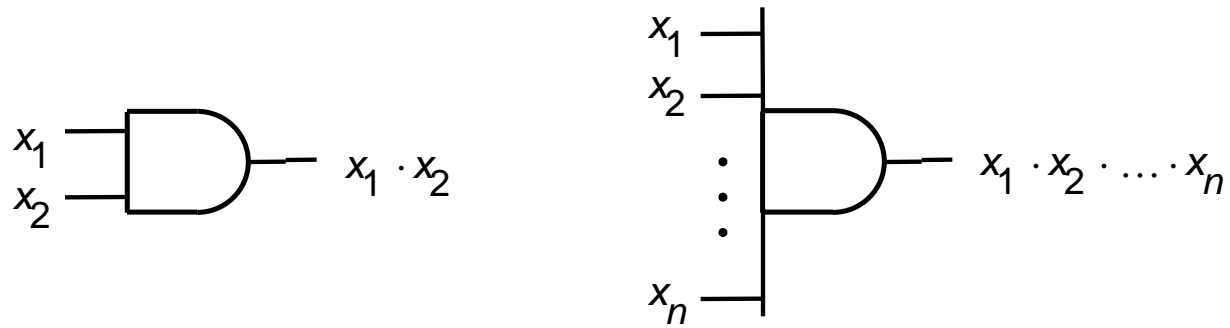- Symbol
 - Closing single quote '
 - Also overline $\overline{\quad}$ and ! symbol
 - Example: x' , \overline{x} , $!x$
- Calling
 - x complement
 - “not of x ”
 - Simpler: “ x bar”




(a) AND gates

Symbols

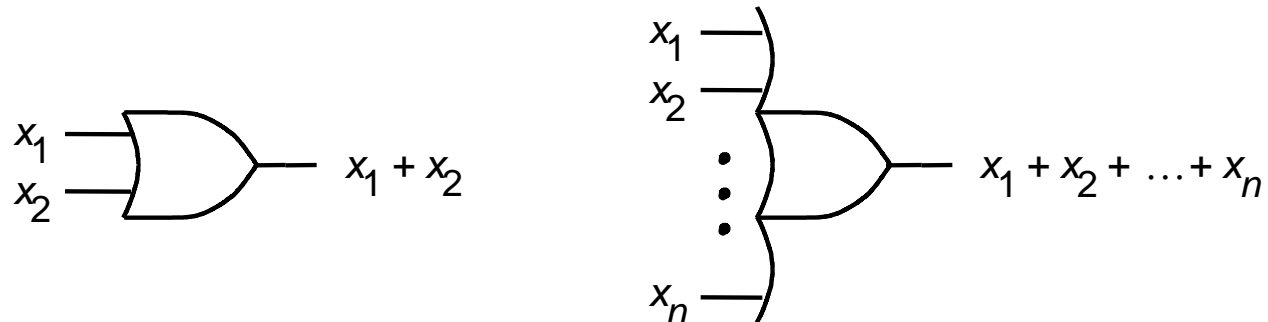

(b) OR gates

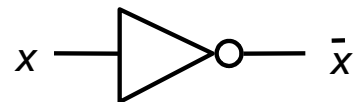

(c) NOT gate

Boolean Algebra

- Named after George Boole

- Axioms

- $0 \cdot 0 = 0$

- $0 + 0 = 0$

- $0' = 1$

- Duality

- $1 \cdot 1 = 1$

- $1 + 1 = 1$

- $1' = 0$

- $0 + 1 = 1 + 0 = 1$

- $0 \cdot 1 = 1 \cdot 0 = 0$

Single Variable Theorems

■ $x \cdot 0 = 0$

■ $x + 1 = 1$

■ $x \cdot 1 = x$

■ $x + 0 = x$

■ $x \cdot x = x$

■ $x + x = x$

■ $x + !x = 1$

■ $x \cdot !x = 0$

■ $x \cdot x \cdot x \cdot \dots x = x$

■ $!!x = x$

Two Variable Theorems

- $x \cdot y = y \cdot x$
- $x + y = y + x$
- Both are commutative

Three Variable Theorems

■ Associative Laws

$$\square \quad x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$\square \quad x + (y + z) = (x + y) + z$$

■ Distributive Law

$$\square \quad x \cdot (y + z) = (x \cdot y) + (x \cdot z)$$

$$\square \quad x + (y \cdot z) = (x + y) \cdot (x + z)$$

■ More as we go



End of Week 1: Module 2

Thank You