

Spring 2015

Week 2 Module 8

Digital Circuits and Systems

Karnaugh Maps

*Shankar Balachandran**


Associate Professor, CSE Department
Indian Institute of Technology Madras

*Currently a Visiting Professor at IIT Bombay


Karnaugh Maps

- Truth tables are a convenient form to represent equations but they don't aid in the simplification of logic equations.
- *Karnaugh maps (K-maps)* are similar to TT's and they lead to graphical methods for boolean expression simplification.
- A K-map is a multi-dimensional tabulation of function values.
- Each *minterm* is assigned an entry (a *cell*) in the table. The cell contains the value of the function for the corresponding minterm.


■ 1 variable K-map: $f(a)$

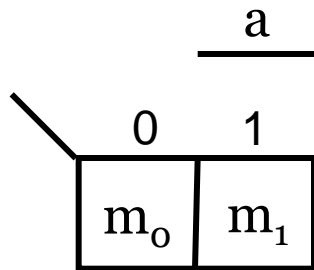


OR

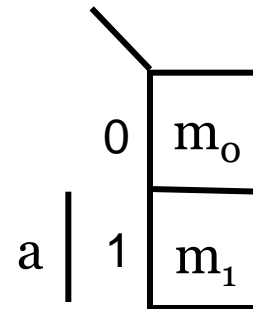

■ 2 variable K-map: $f(a,b)$

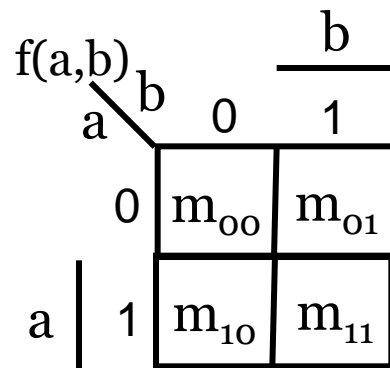

OR

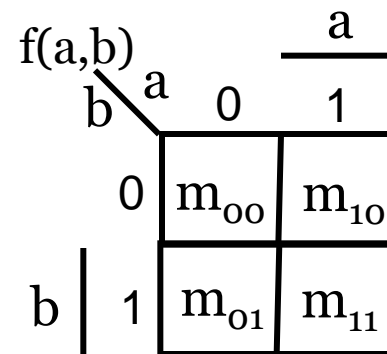

■ 3-variable K-map: $f(a,b,c)$

$f(a,b,c)$

		b			
		bc			
a	0	00	01	11	10
	1	00	01	11	10
		c			

m_{000}	m_{001}	m_{011}	m_{010}
m_{100}	m_{101}	m_{111}	m_{110}

OR

$f(a,b,c)$

		a			
		ab			
c	0	00	01	11	10
	1	00	01	11	10
		b			

m_{000}	m_{010}	m_{110}	m_{100}
m_{001}	m_{011}	m_{111}	m_{101}

■ 4-variable K-map: $f(a,b,c,d)$

$f(a,b,c,d)$

$ab \backslash cd$		c			
		00	01	11	10
a	00	m_{0000}	m_{0001}	m_{0011}	m_{0010}
	01	m_{0100}	m_{0101}	m_{0111}	m_{0110}
	11	m_{1100}	m_{1101}	m_{1111}	m_{1110}
	10	m_{1000}	m_{1001}	m_{1011}	m_{1010}
		d			

b

OR

$f(a,b,c,d)$

$cd \backslash ab$		a			
		00	01	11	10
c	00	m_{0000}	m_{0100}	m_{1100}	m_{1000}
	01	m_{0001}	m_{0101}	m_{1101}	m_{1001}
	11	m_{0011}	m_{0111}	m_{1111}	m_{1011}
	10	m_{0010}	m_{0110}	m_{1110}	m_{1010}
		b			

d

K-map Example 1

$$f = a + bc + \bar{d}$$

$f(a,b,c,d)$

		cd			
		00	01	11	10
ab	00	\bar{d}			\bar{d}
	01	\bar{d}		bc	\bar{d}
	11	a \bar{d}	a	a bc	a bc \bar{d}
	10	a \bar{d}	a	a	a \bar{d}

$$f = a + bc + \bar{d}$$

$f(a,b,c,d)$

		cd			
		ab			
		00	01	11	10
00		1 \bar{d}			1 \bar{d}
01		1 \bar{d}		1 bc	1 bc \bar{d}
11	a	1 \bar{d}	a 1	a 1 bc	a 1 bc \bar{d}
10	a	1 \bar{d}	a 1	a 1	a 1 \bar{d}

K-map Example 1'

$f(a,b,c,d)$

$f = a + bc + \bar{d}$

		ab			
cd		00	01	11	10
00		\bar{d}	\bar{d}	a \bar{d}	a \bar{d}
	01			a	a
	11		bc	a bc	a
	10	\bar{d}	bc \bar{d}	a bc \bar{d}	a \bar{d}

Note: This K-map is drawn by swapping the placement of variable pairs ab and cd

$$f = a + bc + \bar{d}$$

$f(a,b,c,d)$

		ab			
		00	01	11	10
cd	00	$\mathbf{1} \bar{d}$	$\mathbf{1} \bar{d}$	a $\mathbf{1} \bar{d}$	a $\mathbf{1} \bar{d}$
	01	$\mathbf{0}$	$\mathbf{0}$	a $\mathbf{1}$	a $\mathbf{1}$
	11	$\mathbf{0}$	bc $\mathbf{1}$	a bc $\mathbf{1}$	a $\mathbf{1}$
	10	$\mathbf{1} \bar{d}$	bc $\mathbf{1} \bar{d}$	a bc $\mathbf{1} \bar{d}$	a $\mathbf{1} \bar{d}$

K-map Example 2

$$f(w,x,y,z) = w\bar{z} + x\bar{y} + \bar{x}$$

$f(w,x,y,z)$

		yz			
		00	01	11	10
wx	00				
	01				
	11				
	10				

K-map Example 2

$$f(w,x,y,z) = w\bar{z} + x\bar{y} + \bar{x}$$


$f(w,x,y,z)$

		yz					
		wx		00	01	11	10
yz	00	1 \bar{x}	1 \bar{x}	1 \bar{x}	1 \bar{x}		
	01	1 $x\bar{y}$	1 $x\bar{y}$				
	11	$w\bar{z}$ 1 $x\bar{y}$	1 $x\bar{y}$			$w\bar{z}$ 1	
	10	$w\bar{z}$ 1 \bar{x}	1 \bar{x}	1 \bar{x}	1 \bar{x}		$w\bar{z}$ 1 \bar{x}

K-Map Properties

- Minterms mapped to any *two adjacent cells* differ in *exactly one bit* position

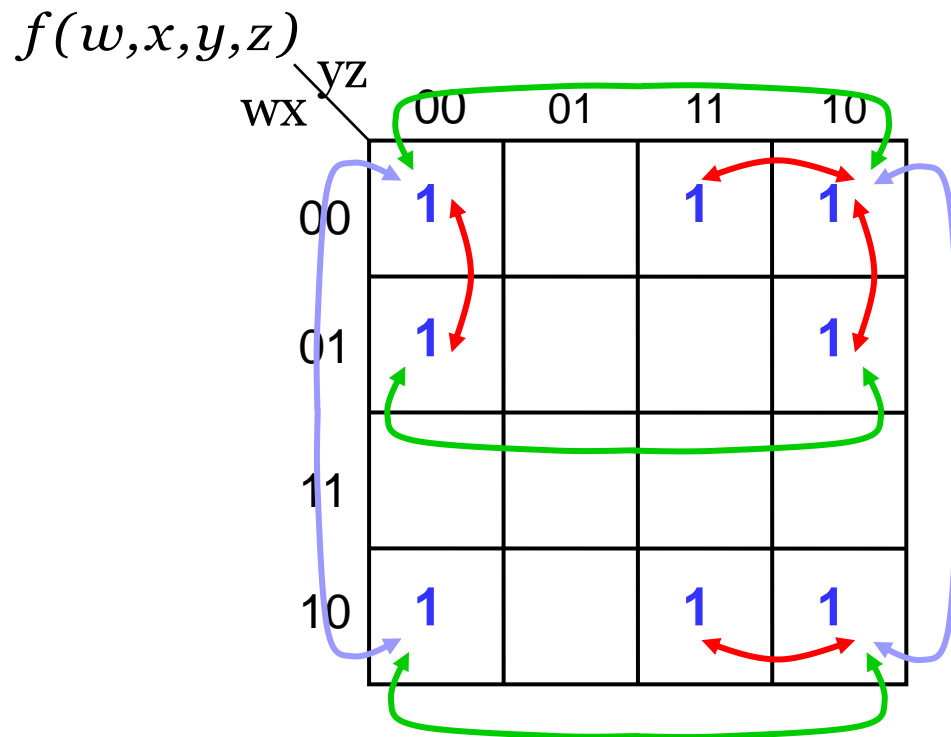Example $f(w,x,y,z) = \sum(0,2,3,4,6,8,10,11)$



- The *sum of two minterms in adjacent cells* can be simplified to a single *product (AND) term with one less variable*.

Example

$f(a,b,c)$

		bc			
	a	00	01	11	10
0		1		1	1
1		1			1

If we combine adjacent minterms in the first column we get,

$$\bar{a}\bar{b}\bar{c} + a\bar{b}\bar{c} = \bar{b}\bar{c}(\bar{a} + a) = \bar{b}\bar{c}$$

That is, variable **a** is eliminated.

Example

$f(a,b,c)$

a \ bc	bc			
	00	01	11	10
0	1		1	1
1	1			1

If we combine adjacent minterms like what is shown above we get,

$$\overline{a}bc + \overline{a}b\overline{c} = \overline{a}b(\overline{c} + c) = \overline{a}b$$

That is, variable **c** is eliminated.



End of Week 2: Module 8

Thank You