

Spring 2015

Week 1 Module 3

Digital Circuits and Systems

Boolean Theorems

*Shankar Balachandran**

Associate Professor, CSE Department
Indian Institute of Technology Madras

*Currently a Visiting Professor at IIT Bombay

DeMorgan's Theorem

$$\overline{(X_1 + X_2 + \dots + X_n)} = \overline{X_1} \cdot \overline{X_2} \cdot \dots \cdot \overline{X_n}$$

$$\overline{(X_1 \cdot X_2 \cdot \dots \cdot X_n)} = \overline{X_1} + \overline{X_2} + \dots + \overline{X_n}$$

Remember:

$$\overline{X \cdot Y} \neq \overline{X} \cdot \overline{Y}$$

$$\overline{X + Y} \neq \overline{X} + \overline{Y}$$

Proof Techniques (Example 1)

■ Prove $x + (y \cdot z) = (x + y) \cdot (x + z)$

$$\begin{aligned}\text{RHS} &= x \cdot (x+z) + y \cdot (x+z) \\ &= x \cdot x + x \cdot z + y \cdot x + y \cdot z \\ &= x \cdot (1+z+y) + y \cdot z \\ &= x \cdot (1) + y \cdot z \\ &= x + y \cdot z\end{aligned}$$

Fairly Straightforward

Proof Techniques (Example 2)

■ Prove $x + x \cdot y = x$

$$\begin{aligned}x + x \cdot y &= x \cdot 1 + x \cdot y \\&= x \cdot (1 + y) \\&= x \cdot 1 \\&= x\end{aligned}$$

Introduce a constant

Proof Techniques (Example 3)

■ Prove $x.y + y.z + x'.z = x.y + x'.z$

$$\begin{aligned}\text{LHS} &= x.y + y.z.1 + x'.z \\ &= x.y + y.z.(x+x') + x'.z \\ &= x.y + y.z.x + y.z.x' + x'.z \\ &= x.y(1+z) + (y+1).x'.z \\ &= x.y + x'.z\end{aligned}$$

Introduce a constant and introduce a function

Boolean Techniques (Example 4)

■ Simplify $x.y + x.y.z + y.z$

$$\begin{aligned}\text{LHS} &= x.y + x.y.z + y.z \\ &= x.y + x.y.z + x.y.z + y.z \\ &= x.y (1 + z) + y.z (x + 1) \\ &= x.y + y.z \\ &= y.(x+z)\end{aligned}$$

Introduced a copy of a term

A simpler derivation is there. Think about it!

Exercise :

Prove the Two Variable Theorems Below

■ Absorption

$$\square \quad x + (x \cdot y) = x$$

$$\square \quad x \cdot (x + y) = x$$

■ Combining

$$\square \quad x \cdot y + x \cdot y' = x$$

$$\square \quad (x + y) \cdot (x + y') = x$$

■ DeMorgan's Laws (You probably know how to use Venn Diagram to prove this)


$$\square \quad (x + y)' = x' \cdot y'$$

$$\square \quad (x \cdot y)' = x' + y'$$


$$\square \quad x + (x' \cdot y) = x + y$$

$$\square \quad x \cdot (x' + y) = x \cdot y$$

Boolean Functions

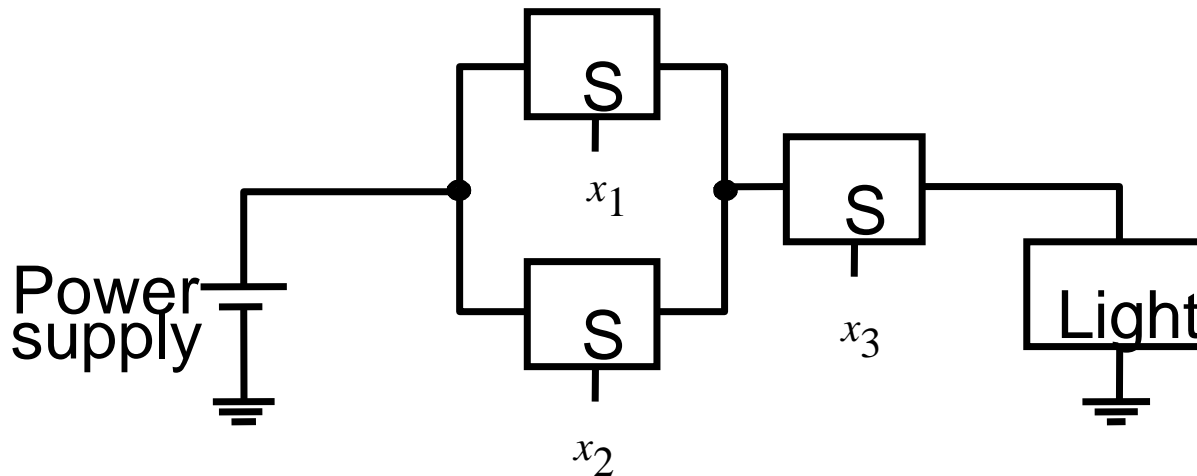

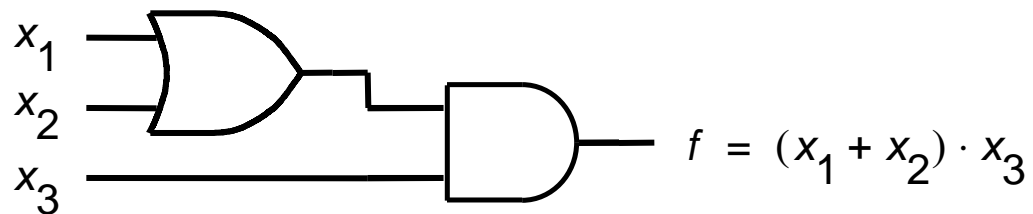
$$\begin{aligned} f &= (x_1 \text{ OR } x_2) \text{ AND } (x_3) \\ &= (x_1 + x_2) \cdot x_3 \end{aligned}$$



Design Problem 1

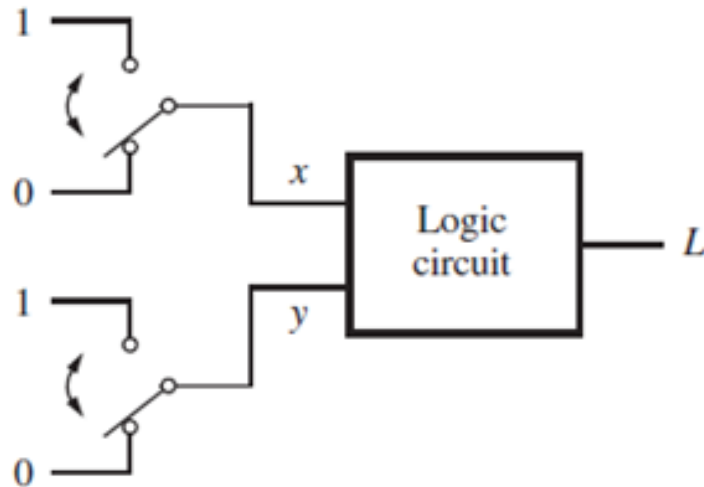- Design a circuit for staircase light control using a two-way switch
- If both switches are OFF or ON, light is off
- If one of them is ON and another is OFF, the light is ON




(a) Two switches that control a light

x	y	L
0	0	0
0	1	1
1	0	1
1	1	0

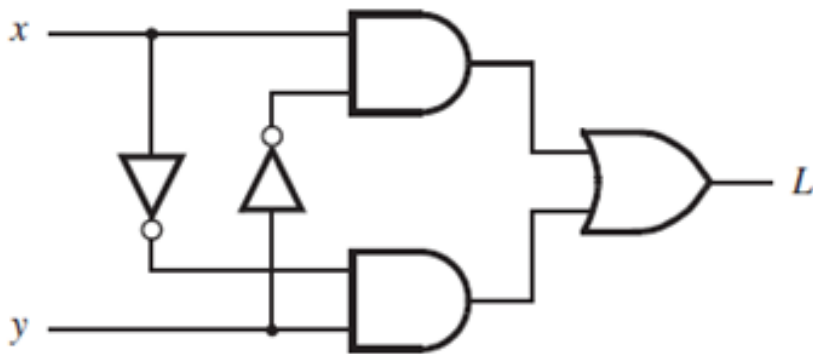(b) Truth table

Boolean Expression

- Lamp is ON when
 - Either x is ON and y is OFF
 - Or x is OFF and y is ON
- $L = x \cdot y' + x' \cdot y$



(c) Logic network



(d) XOR gate symbol

Design Problem 2


- Design a circuit which realizes the following truth table

x_1	x_2	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

$f = ?$


Design Problem 2 (contd.)

■ $f = x_1'.x_2' + x_1'.x_2 + x_1.x_2$

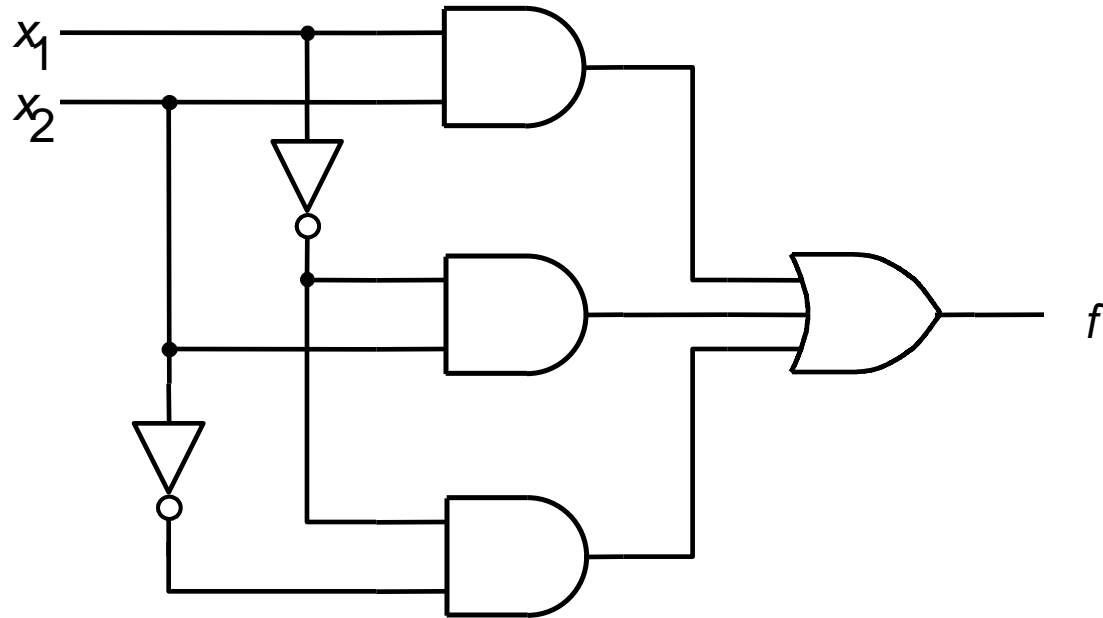

Power of Simplification
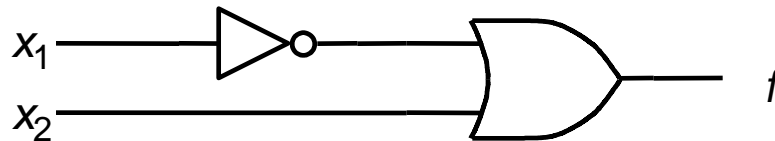
$$\begin{aligned} \blacksquare f &= x_1'.x_2' + x_1'.x_2 + x_1.x_2 \\ &= x_1'.x_2' + x_1'.x_2 + x_1'.x_2 + x_1.x_2 \\ &= x_1'.(x_2' + x_2) + (x_1' + x_1).x_2 \\ &= x_1'.1 + 1.x_2 \\ &= x_1' + x_2 \end{aligned}$$



Minimal-cost realization

Positional Number System

■ Decimal: Uses base 10

Note: base 10 →

$\times 10^2$	$\times 10^1$	$\times 10^0$
7	5	6

Hundreds Tens Ones

First column starts at "1"

$$= 7 \times 10 \times 10 + 5 \times 10 + 6 \times 1$$

■ Binary Number: Uses base 2

Note: base 2 →

$\times 2^2$	$\times 2^1$	$\times 2^0$
1	1	1

$$= 1 \times 2 \times 2 + 1 \times 2 + 1 \times 1$$

2^2 2^1 2^0

Binary to Decimal

- Because humans work well with decimal, it is useful to know how to convert between binary and decimal:

$$0000_2 = 0$$

$$0001_2 = 1$$

$$0010_2 = 2$$

$$0011_2 = 3$$

$$0100_2 = 4$$

$$0101_2 = 5$$

$$0110_2 = 6$$

$$0111_2 = 7$$

$$1000_2 = 8$$

$$1001_2 = 9$$

$$1010_2 = 10$$

$$1011_2 = 11$$

$$1100_2 = 12$$

$$1101_2 = 13$$

$$1110_2 = 14$$

$$1111_2 = 15$$

Binary to Decimal (contd.)

8	4	2	1
1	1	0	1

$$= 1 \times 8 + 1 \times 4 + 1 \times 1 = 8 + 4 + 1 = 13$$

To convert to decimal, represent the column values in decimal

128	64	32	16	8	4	2	1
1	0	0	1	1	1	0	1

$$=$$

$$1 \times 128 + 1 \times 16 + 1 \times 8 + 1 \times 4 + 1 \times 1 = 128 + 16 + 8 + 4 + 1 = 157$$



End of Week 1: Module 3

Thank You